

Fundamentals of Digital Design

A story of how mathematics, logic and physical transistors combine to create computers.

Written and illustrated by Michelle Phung

2013

Digital Design / Binary Number System

The language of computers is written in binary code.

In the same way we use the letters 'C', 'A', and 'R' to represent the word 'car', and the word 'car' to represent the concept of the automobile, computers use '0's and '1's to represent words, instructions, rules, everything. The two states describe an entire world of software.

For example,

if you can imagine that the numbers,
1000011 represent the letter 'C',
and 1000001 represent 'A',
and 1010010 represent 'R',
then you can start to imagine how binary code work.

Since binary is so simple (only two options '0' or '1'),
the chance of misinterpreting signals is low,
and as a result, there are less likely to be errors.

Let's start with how to read binary.

Digital Design / Binary Number System

The system that most of us are familiar with is the base 10 system (i.e., 1 2 3 4 5 6 7 8 9 0), also called decimal.

Base 16 system has 16 symbols (0 1 2 3 4 5 6 7 8 9 A B C D E F) and is also called hexadecimal.

There are only two numbers in the binary numbering system: '0' and '1'.

It is a base 2 system.

There are several ways to show what base a number is in:

sometimes a letter,

0x32 is in hexadecimal,

0b110010 is in binary,

(decimal is most used, so it doesn't have a special letter notation)

or a subscript,

32₁₆ is in hexadecimal (base 16)

110010₂ is in binary (base 2)

50₁₀ is in decimal (base 10)

is shown to clarify which base is being used.

Since there are only two numbers to work with, we have to interpret the value of the number by the position of the numbers.

$$001_2 = 1_{10}$$

$$010_2 = 2_{10}$$

$$011_2 = 3_{10}$$

Digital Design / Binary Number System

Since decimal is the easiest to understand, let's start by figuring how to convert binary into decimal.

First, realize that for every position left of the number, the value of that number increases by 2^n .

The numbers in blue are in base 10.

We multiply them by their position, and add the sum to get the number in decimal.

The first position (red circle) is to be multiplied by 2^0 .

The second position (orange circle) is to be multiplied by 2^1 .

The third position (yellow circle) is to be multiplied by 2^2 .

If there was a fourth position, it would be multiplied by 2^3 , and if there was a fifth position, it would be multiplied by 2^4 .

1 0 0₂ = 4₁₀


$2^0 \times 0$


$2^1 \times 0$


$2^2 \times 1$


Digital Design / Binary Number System

 
Once we get the products (0, 0, and 4), from the positions, we add them all together, and the resultant sum is the converted value in decimal.



 

 

 

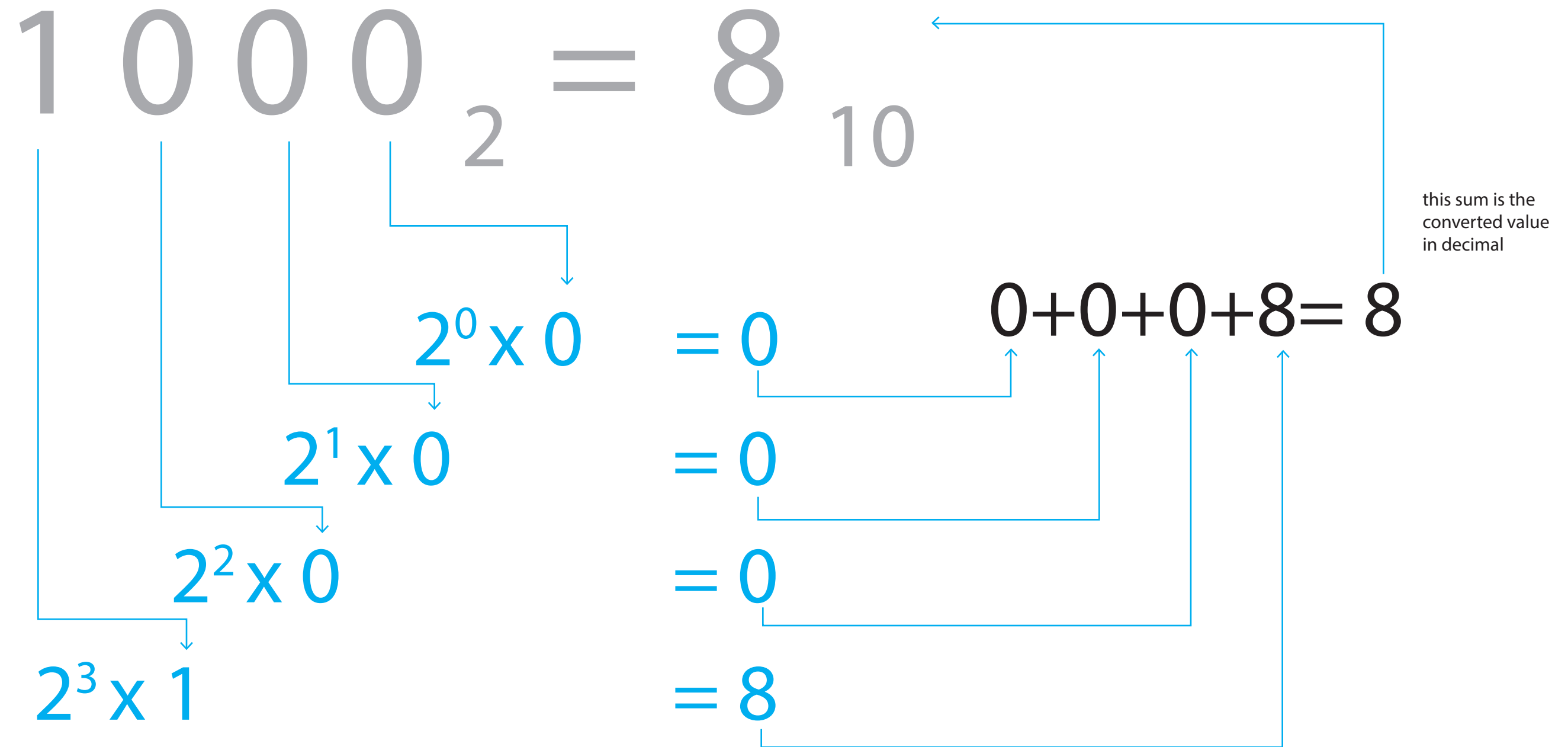


Digital Design / Logic Gates

The special nature of the binary numbering system gives way to a subdivision of algebra, called Boolean algebra (also known as Boolean Logic).

Since there are only two numbers in the binary numbering system, it lends itself to other interpretations. The two numbers, '0' and '1' can represent states, like on and off, true and false, or HIGH and LOW.

 
Boolean algebra has its own rules, notations, and operations. There are three basic operations, AND, OR, and NOT.



This is the AND gate symbol.

The gates pictured to the right are symbols that represent Boolean algebra operations. Similar to a plus or minus symbol, they represent an operation taking place that produces a single result.

 
These gates also represent physical electrical components, which can be used to build and control circuits, and which, in turn can be used to build complex computer systems.



This is the OR gate symbol.

The gates have inputs on the left hand side. The AND and OR gates pictured here take 2 inputs each, and result in one output.

 The NOT gate takes one input (on the left hand side), and results in one output (on the right hand side).




This is the NOT gate symbol.

Digital Design / Logic Gates - AND, OR, NOT


There are more logic gate symbols and operations, but these are the basics.
To gain an idea of how the AND, OR, and NOT operations work, let us consider that '0' is 'false' and '1' is 'true'.



 The AND gate outputs a true result only if both of the inputs are true. Otherwise, the result is false.



 The OR gate outputs a true signal in cases where either one of the inputs are true. It's output is only false when both inputs are false.



The NOT gate outputs the opposite of the input.

Truth Tables can quickly show the result of an operation on the inputs.
Each operation has it's own truth table. Logic gates can have more than two inputs but the most shown here are two. For larger gates that have more than two inputs, a different truth table has to be made, but the rules stay the same in each case.

input x	input y	output z	
0	0	0	if the x input is 0 and the y input is 0, then the result is 0
0	1	0	if the x input is 0 and the y input is 1, then the result is 0
1	0	0	if the x input is 1 and the y input is 0, then the result is 0
1	1	1	if the x input is 1 and the y input is 1, then the result is 1

input x	input y	output z
0	0	0
0	1	1
1	0	1
1	1	1


input	output
0	1
1	0

Digital Design / Logic Gates - NAND, NOR, XOR, XNOR




The NAND gate outputs a false result only if both of the inputs are true. Otherwise, the result is true.

input x	input y	output z
0	0	1
0	1	1
1	0	1
1	1	0

 


The NOR gate outputs a true signal in cases when both inputs are false. Otherwise, the result is false.

input x	input y	output z
0	0	1
0	1	0
1	0	0
1	1	0

 

The XOR gate outputs a true signal if the inputs are not the same.

input x	input y	output z
0	0	0
0	1	1
1	0	1
1	1	0

 


The XNOR gate outputs a true signal if both inputs are the same.

input x	input y	output z
0	0	1
0	1	0
1	0	0
1	1	1

Digital Design / Integrated Circuits

 
Chips in computers are simply these logic gates, arranged in a specific way, in order produce a desired output.



Pictured above (on the left) is a Texas Instrument SN74LS08 integrated circuit, which houses 4 AND gates within it.

This integrated circuit (aka IC chip or a microchip) shown is actually pretty big, relatively speaking. The ICs used in computers, calculators, and smart phones are much, much smaller.

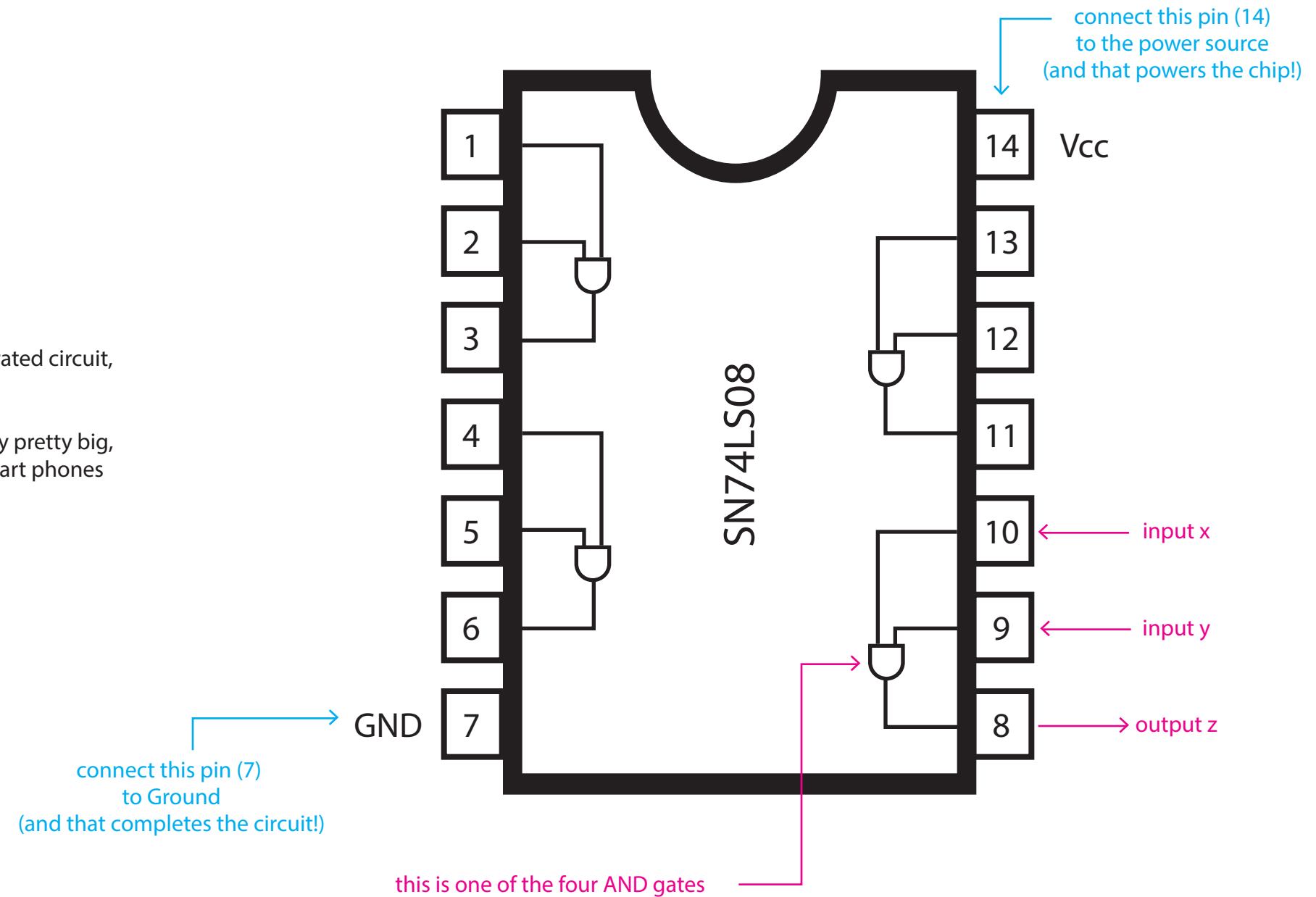The inside connections are pictured on the right.



Digital Design / Half-Adder

A basic circuit is a half-adder. It adds two (one digit) numbers.

The significance of a half adder being able to sum two numbers is that addition is an important instruction at a very low level of computing, and thus that importance propagates to higher levels of computing.

Since there are only 2 numbers in the binary system, there are only so many combinations of addition that can occur.

If operand x =0 and operand y =0 then the sum = 0.

If x=0 and y=1 then $0+1=1$ (sum is 1).


If x=1 and y=1 then $1+0=1$ (sum is 1).

If x=1 and y=1 then $1+1=10$ (sum is 10...remember we're in binary)*.

*Please note the special case,
where x=1 and y=1

The trouble with this case is that the output of each logic gate can only have one place, meaning, it is only one digit. The output of the entire half-adder circuit is 2 outputs, with the output of the AND gate acting as the carry, or over flow, when the sum is bigger than one digit.

 When this happens then carry=1 and sum=0, which, in this interpretation can be read as 10, or the correct sum of $1+1=10$.



Digital Design / Multiple Digit Addition

For handling the addition of two 1-bit numbers, the half adder works great. However, the limitation of the half-adder is that it only sums 1-bit numbers.

For addition to be useful, the number of bits must be magnitudes larger. If we take a look at a common method to work out addition, we can start to recognize the issues that a circuit may have.

The order of the steps we take to add two numbers are in blue circles.

1

$$\begin{array}{r} 165 \\ + 237 \\ \hline \end{array}$$

Conventionally the sum is placed here.

2

↓

$$\begin{array}{r} 165 \\ + 237 \\ \hline \end{array}$$

We start with the right most column, where 5+7=12.

3

↓

$$\begin{array}{r} 1 \\ 165 \\ + 237 \\ \hline 2 \end{array}$$

Since 12 has more than one digit, the 1 in the tens place is “carried over” to the next column, to be added into the sum of the next two numbers.

4

↓

$$\begin{array}{r} 11 \\ 165 \\ + 237 \\ \hline 02 \end{array}$$

The addition continues to move left, carrying over as necessary.

5

$$\begin{array}{r} 11 \\ 165 \\ + 237 \\ \hline 402 \end{array}$$

The final sum is 402.

Digital Design / Multiple Bit Addition

Addition in binary works in the same fashion.

The order of the steps we take to add two numbers are in blue circles.

1

↓

$$\begin{array}{r} 10100101 \\ + 11101101 \\ \hline \end{array}$$

We start with the right most column, adding the "least significant bit" (LSB) from each number together.

2

↓

$$\begin{array}{r} 10100101 \\ + 11101101 \\ \hline 0 \end{array}$$

In binary, 1+1=10. 10 has two places, so the 1 is carried over to next column.

3

↓

$$\begin{array}{r} 10100101 \\ + 11101101 \\ \hline 10 \end{array}$$

The 1 that was "carried over" to the next column, is added into the sum of the next column, 0+0+1=1.

4

↓

$$\begin{array}{r} 10100101 \\ + 11101101 \\ \hline 010 \end{array}$$

The addition continues to move left, carrying over as necessary.

5

↓

$$\begin{array}{r} 1111111 \\ 10100101 \\ + 11101101 \\ \hline 110010010 \end{array}$$

The final sum is 110010010.

Notice that while the two addends have 8 bits each (8 bits = 1 byte), the sum has 9 bits in it.

This extra 9th bit is the leftmost bit, and the left most bit is called the most significant bit (MSB)*.


*When the left most bit = MSB, we are using in "Big Endian" notation.

In "Little Endian" notation the left most bit would be the LSB.

Digital Design / Full Adder

One could imagine that chaining multiple half-adders together could produce our desired output for a multi-bit sum. However, this concept of “carrying over” is not considered when using just the half-adder.

 This is where the full adder comes into play. The full-adder has an extra input called the ‘carry in’ or commonly denoted by ‘ C_{in} ’.



Digital Design / Carry In and Carry Out

Look at the earlier addition diagram:

10100101

+ 11101101

notice this phantom row that gets dynamically filled with 1s as the resultant sum from the previous columns addition takes place

This 'phantom row' is the row in which all the carry in's get placed. When a column has a carry over (1) on top of it, the result of that row is the sum of 3 numbers: the two in that column from the original two numbers, plus the additional carry over.

Let's make some distinctions between carry in and carry out:

The carry in is the 1 that is added to the next column of numbers,

While the carry out is the 1 that is the result of the sum of a column.

1

10100101

+ 11101101

10

this '1' is the carry out of the right most column

it is also the carry in of the next column

The addition of a third addend means that there are more combinations of addition.

Note that because of the nature of the binary system, for n.inputs, we know there are 2^n unique combinations for inputs.

A truth table for a full.adder reveals how the carry in can influence the result:

input A	input B	carry in	carry out	sum bit
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

*notice the sum of these bits are represented here in binary

input A		input B		carry in		carry out		sum bit
0	+	0	+	0	=	0		0
0	+	0	+	1	=	0		1
0	+	1	+	0	=	0		1
0	+	1	+	1	=	1		0
1	+	0	+	0	=	0		1
1	+	0	+	1	=	1		0
1	+	1	+	0	=	1		0
1	+	1	+	1	=	1		1

It may help to imagine 'plus' and 'equal' signs in this truth table.

Digital Design / Multiple Bit Addition Redux - Part 1

Let's take a look at binary addition again, this time keeping notice of the carry ins and carry outs.

1

0

1

1

1

1

0

0

1

0

1

input A →

input B → +

11101101

input A	input B	carry in	carry out	sum bit
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

We begin with the right most column, and this time, we can look at how reading the truth table could help us.

This column has :
1 for input A and
1 for input B, and
0 carry in.

This 1 narrows down the table to the last 4 rows

This 1 narrows the table down further, we know that the row we want is in the last 2 rows

This 0 is implied (since it's the first row), so the carry in = 0. This narrows down the table to the desired row.

2

1

1

0

0

1

0

1

0

1

0

10100101

+ 11101101

0

input A	input B	carry in	carry out	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

The row (in the truth table) that matches our inputs on the left side, gives the result on the right side.

It says that the sum is 0, and the carry out is 1.

This carry out goes on top of the next column.

Digital Design / Multiple Bit Addition Redux - Part 2

3

1

input A → 10100101

input B → + 11101101

0

To reiterate:
the 1 that was “carried over”
to the next column, is added
to the sum of the next column.

Now we do addition to the
next column (indicated above
with the blue arrow).

Again, we can use the truth table,
but realize that the carry out from
the last computation, is now the
carry in this addition.

input A	input B	carry in	carry out	sum bit
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

4

01

10100101

+ 11101101

10

From the truth table,
the sum bit = 1 ,
(0+0+1=1),
and the carry out bit = 0.

This continues left, carrying
over as necessary. When
the carry out bit = 0,
it is usually omitted, and
understood that ‘nothing’
is added.

5

111 11 1

10100101

+ 11101101

110010010

The final sum is 110010010.

Digital Design / 4-bit Adder Introduction


Building 4 bit adder gives context to how adders work in a system.

A 4-bit adder adds two 4-bit numbers. It has four, and only four, places in each number. This means that the minimum number that one of the addends can be is 0000. The maximum an addend can be is 1111_2 . (recall: $1111_2 = 15_{10}$)


An example:

A=1101
B=1001

 Since the adder is going to sum the LSB of A with the LSB of B, and then every corresponding bits after that, it is common to name each bit.



Similarly for B:

 

So when we add them together, roughly, it would look something like this:

Carry out ₃	Carry out ₂	Carry out ₁	Carry out ₀	0
0	A ₃	A ₂	A ₁	A ₀
+ 0	+ B ₃	+ B ₂	+ B ₁	+ B ₀
Carry out ₃	Sum ₃	Sum ₂	Sum ₁	Sum ₀

Notice that the “carry-outs” are the “carry-ins” for the next column.

It may help to realize:

Carry in₁=Carry out₀

Carry in₂=Carry out₁

Carry in₃=Carry out₂

Carry in₄=Carry out₃

and this is the final carry out, it represents the MSB of the sum, it is exceptional because for adding two numbers with 4 places (4-bits), the sum can be a 5-bit number (it has 5 places).

Digital Design / 4-bit Adder - Each Bit Counts

Revisiting the full adder again:

And the previous equations:

Carry out₃

0

+

0

Carry out₃

Carry out₂

A₃

+

B₃

Sum₃

Carry out₁

A₂

+

B₂

Sum₂

Carry out₀

A₁

+

B₁

Sum₁


0

A₀

+

B₀

Sum₀

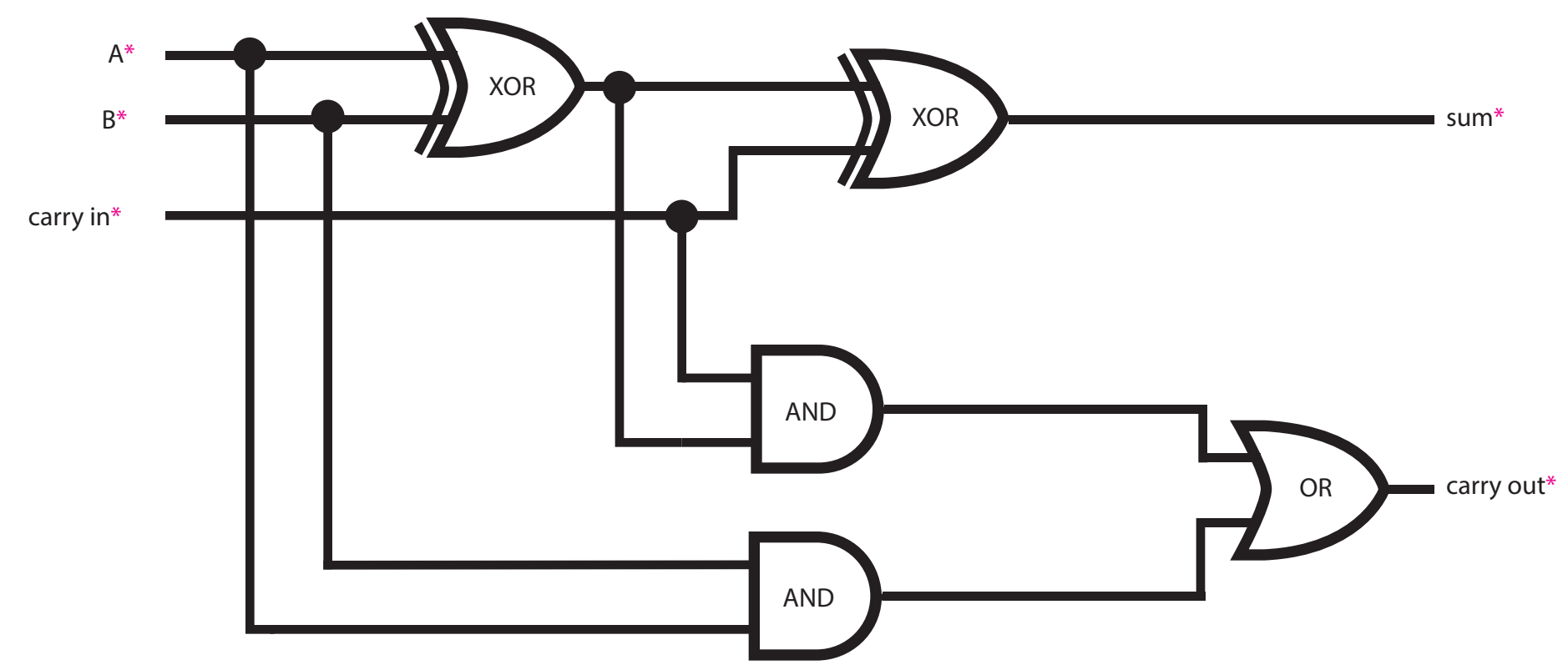


*Note that each of the inputs and outputs are 1 bit signals.

Paired with each equation, we would need 4 full adders to create the 5-bit wide sum (C_{out}, Sum₃, Sum₂, Sum₁, Sum₀).

Digital Design / 4-bit Adder - Ripple Carry

All together now:

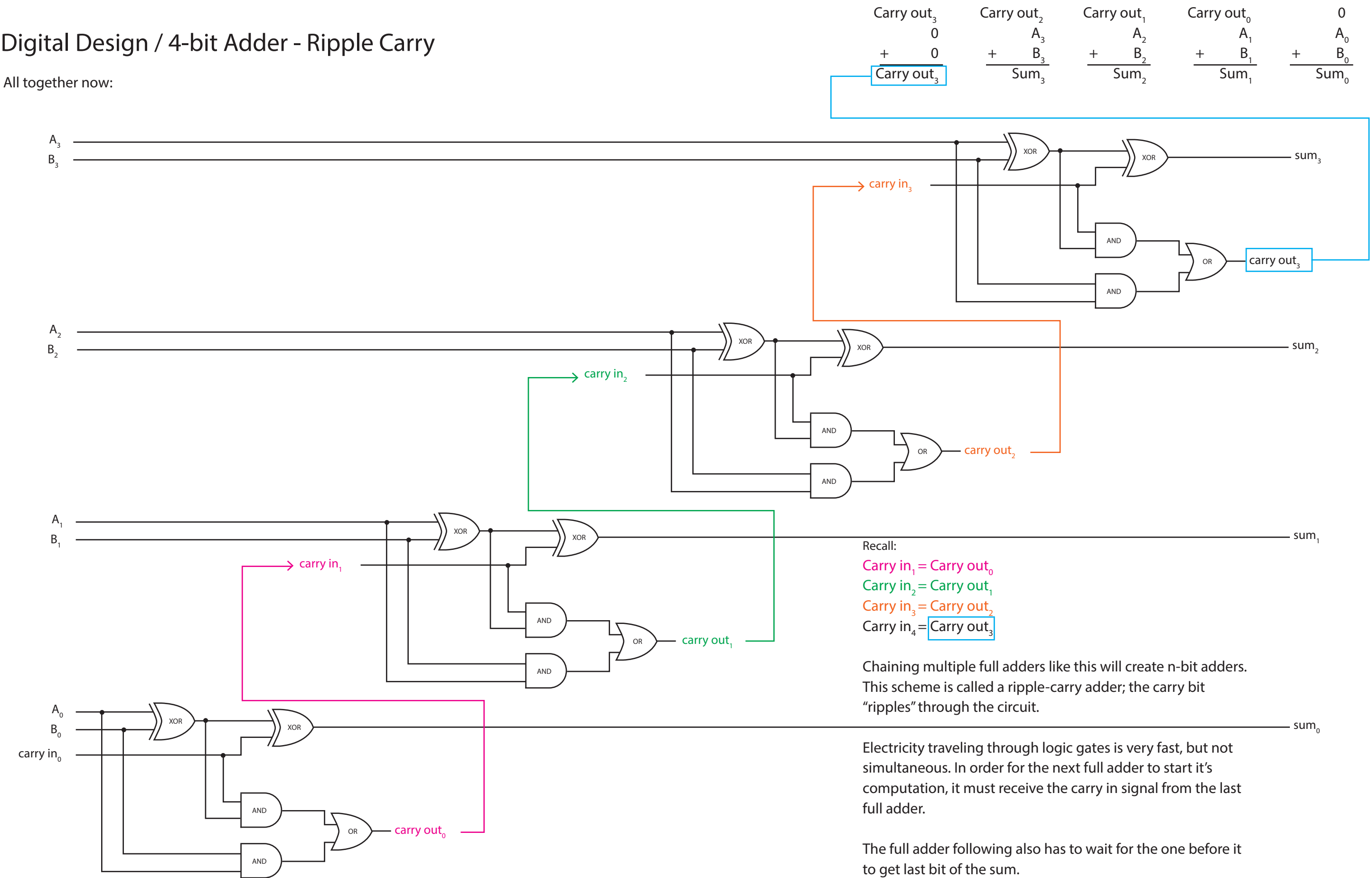

Recall:
Carry in₁ = Carry out₀
Carry in₂ = Carry out₁
Carry in₃ = Carry out₂
Carry in₄ = Carry out₃

Chaining multiple full adders like this will create n-bit adders. This scheme is called a ripple-carry adder; the carry bit “ripples” through the circuit.

Electricity traveling through logic gates is very fast, but not simultaneous. In order for the next full adder to start its computation, it must receive the carry in signal from the last full adder.

The full adder following also has to wait for the one before it to get last bit of the sum. This waiting time is called propagation delay.

Digital Design / 4-bit Adder - Carry Look Ahead

The propagation delay from the time the adder starts obtaining the first carry to the time it gets the last carry out in a ripple carry adder means that for an n-bit adder, the n-th adder must wait n times the propagation delay of one full adder. For example, if there are 64-bit numbers being added together, the last bit and its carry-out would have had to wait 64 times the propagation delay of each of the full adders.

This lag is exacerbated when larger number of bits are being added together.

There are other types of adders. The most efficient currently is called the Carry-Look Ahead Adder. The trade off with the Carry-Look Ahead adder is that it uses many more logic gates than the Ripple-Carry Adder, but is much faster.

The reason that the Ripple-Carry adder is slow is because the carries must ripple through the circuit, one at a time, as this is how the circuit is set up. However, if the circuit could receive all of carries at the same time, then all the bits of the sum would occur at once, instead of obtaining them one bit at a time.

To get all the carry-outs at the same time, we can rely on the following equations:

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 c_1$$

$$c_3 = g_2 + p_2 c_2$$

$$c_4 = g_3 + p_3 c_3$$

Note that all of the equations follow the form: $c_{i+1} = g_i + p_i c_i$
where :

i goes from 1 to 4,

c_0 is the initial carry in,

g_i is called the 'generate' term, obtained from A_i AND B_i

p_i is called the 'propagate' term, obtained from A_i OR B_i

It looks as though each c_{i+1} would depend on c_i , indicating a delay, but since all the p's and g's are received simultaneously, the equations can be expanded:


$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 c_1 = g_1 + p_1 (g_0 + p_0 c_0)$$

$$c_3 = g_2 + p_2 c_2 = g_2 + p_2 (g_1 + p_1 (g_0 + p_0 c_0))$$

$$c_4 = g_3 + p_3 c_3 = g_3 + p_3 (g_2 + p_2 (g_1 + p_1 (g_0 + p_0 c_0)))$$

 Digital Design / 4-bit Adder - Carry Look Ahead Adder



This is a diagram of a Carry-Look Ahead 4-bit Adder.

When there are more bits being added, say in a 16-bit or 32-bit adder, the number of logic gates increases, but it takes the same amount of time to arrive at the sum.